

Electricity

— Flow of electrons

= flows through conductors


— 'Flow restricted by insulators

Resistance, Current, & Voltage

Voltage = Potential difference of electricity

Current = speed of flow

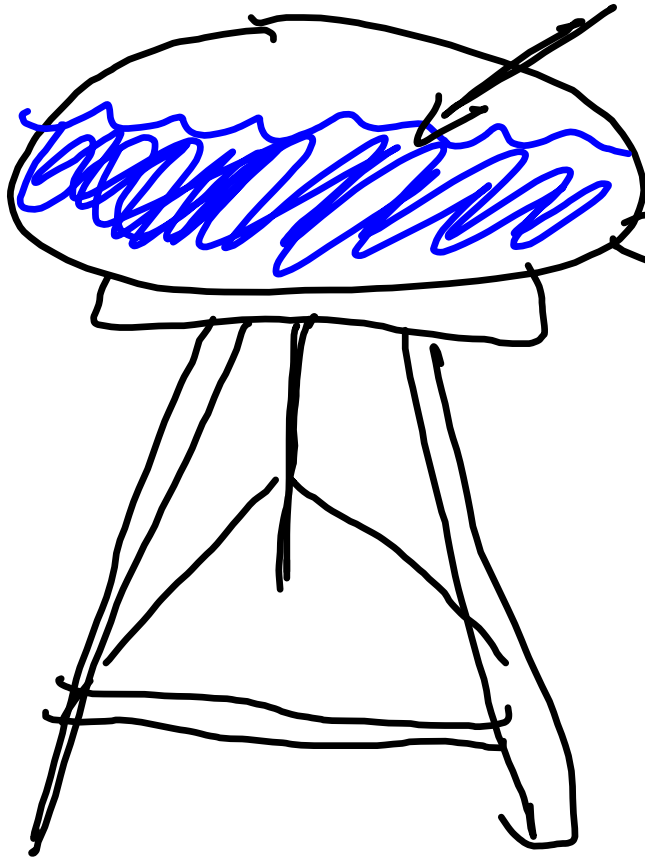Resistance = how much we are restricting flow




Voltage is like the water pressure

Resistance is like the size of pipe




Current



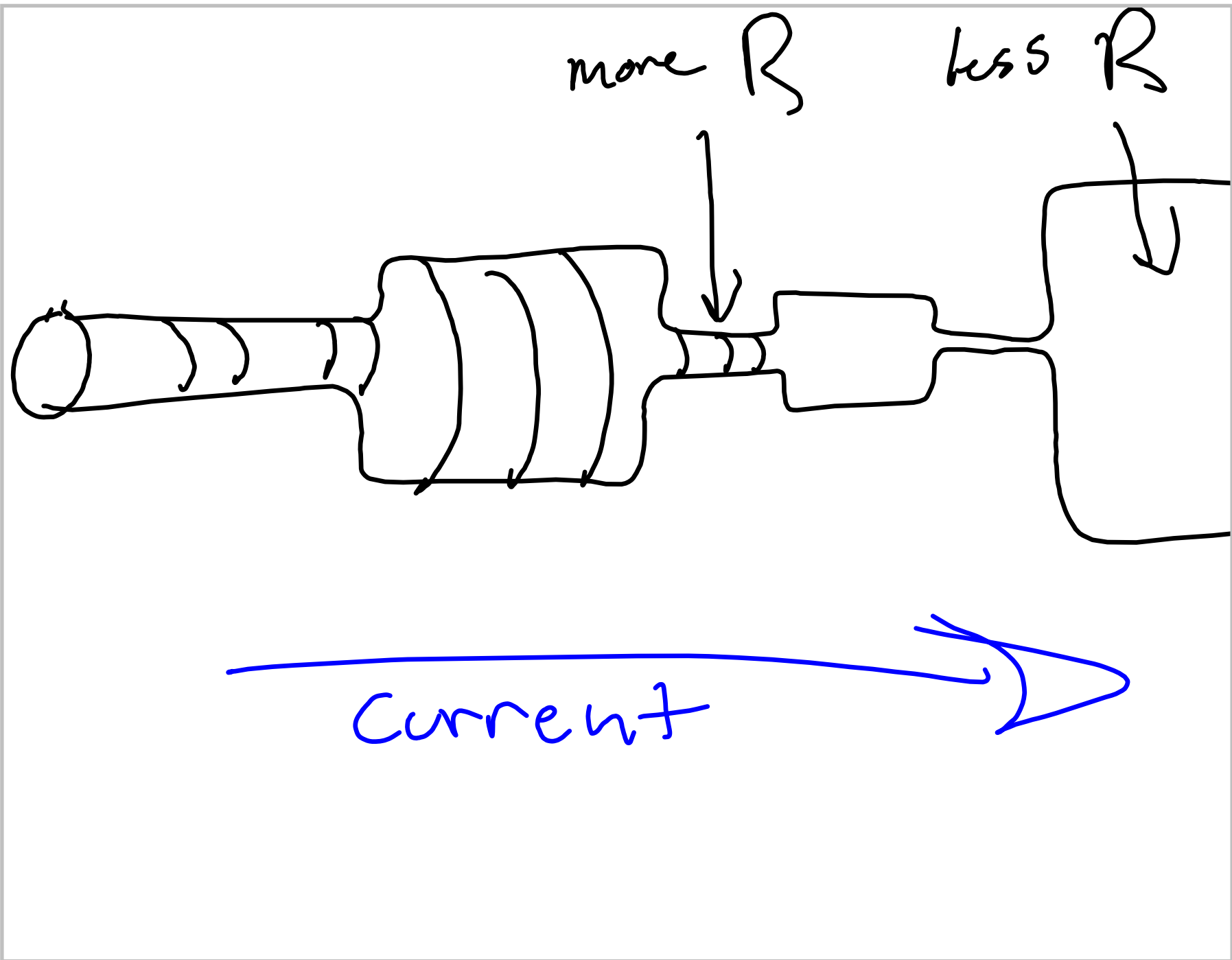

Ohms Law

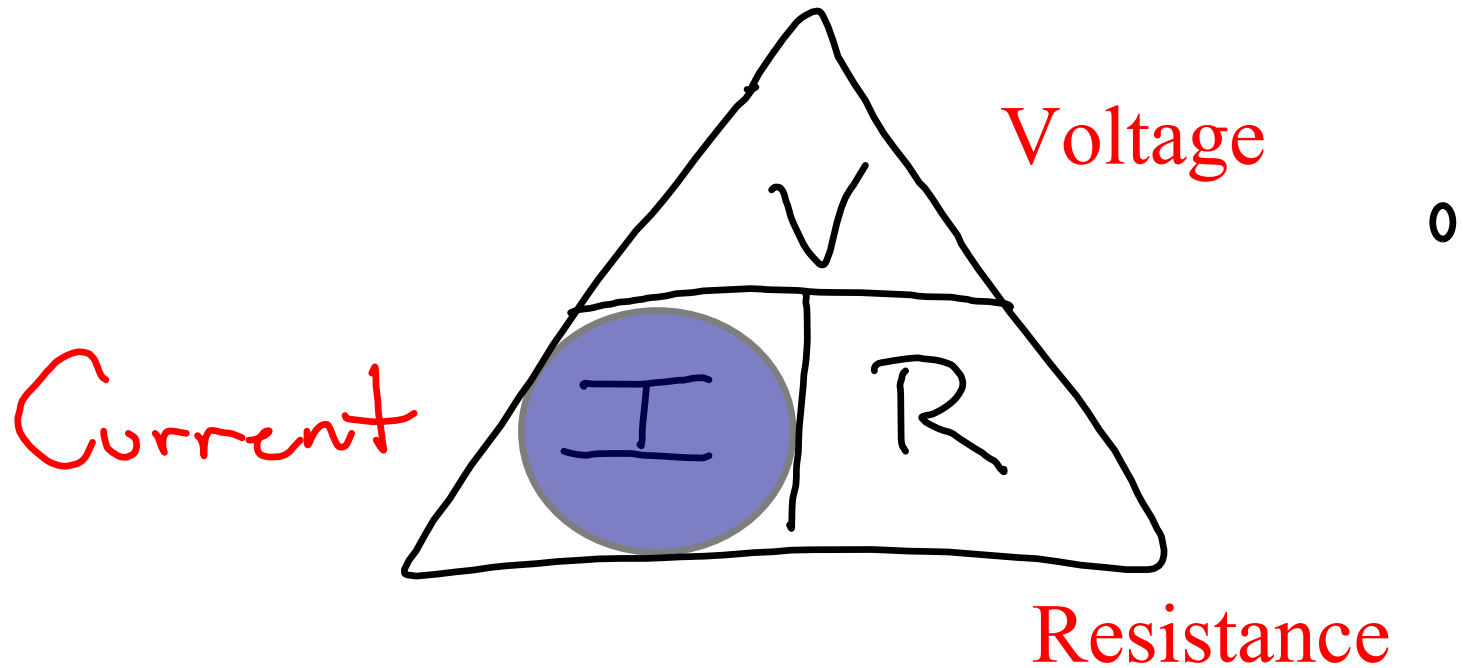

$$V = I \times R \quad \text{VOLTS}$$


Ohms

$$I = \frac{V}{R} \quad \text{Amps}$$

LAW

$$R = \frac{V}{I} \quad \Omega \rightarrow \text{"Ohms"}$$

ex 1.

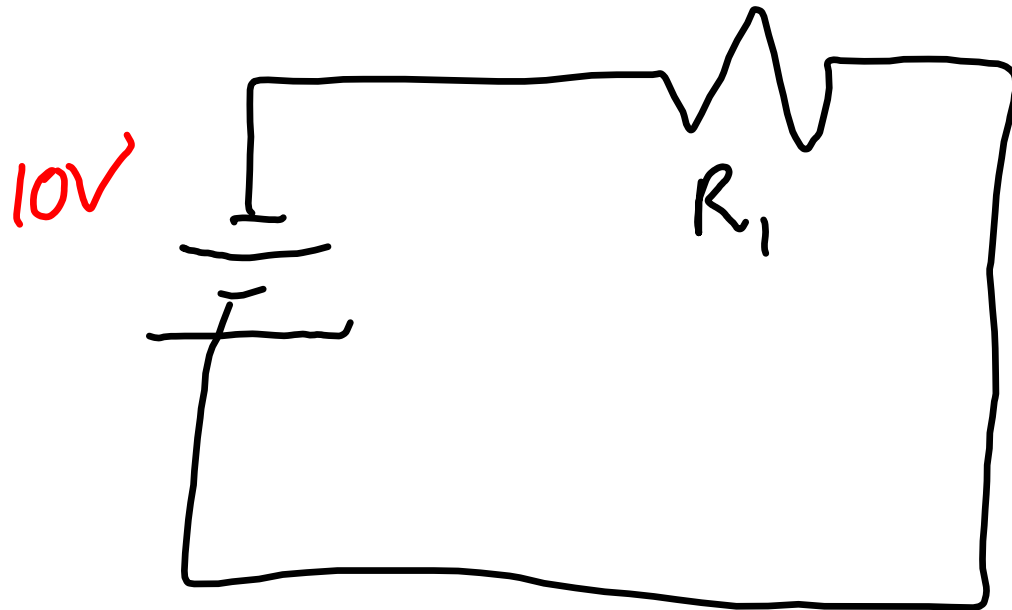


$$R_1 = 200\Omega$$

$$I = \frac{V}{R}$$
$$= \frac{10V}{200\Omega}$$

$$= 0.05 A$$

$$= 50 mA$$

Series Circuits

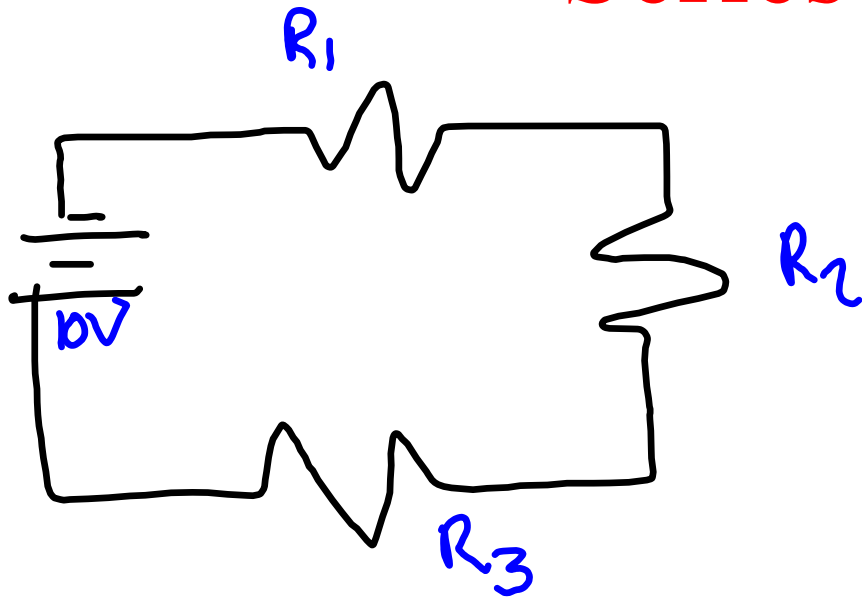

$$\begin{aligned}R_1 &= 100 \Omega \\R_2 &= 330 \Omega \\R_3 &= 700 \Omega\end{aligned}$$

$$V = I \times R$$


$$\begin{aligned}R_{\text{Total}} &= R_1 + R_2 + R_3 \\&= 100 + 330 + 700 \\&= 1130 \Omega\end{aligned}$$

$$\begin{aligned}I &= \frac{V}{R} \\&= \frac{10}{1130} \\&= 0.00884 \text{ A} \\&= 8.84 \text{ mA}\end{aligned}$$

Series Circuits

$$R_2 = 330 \Omega$$

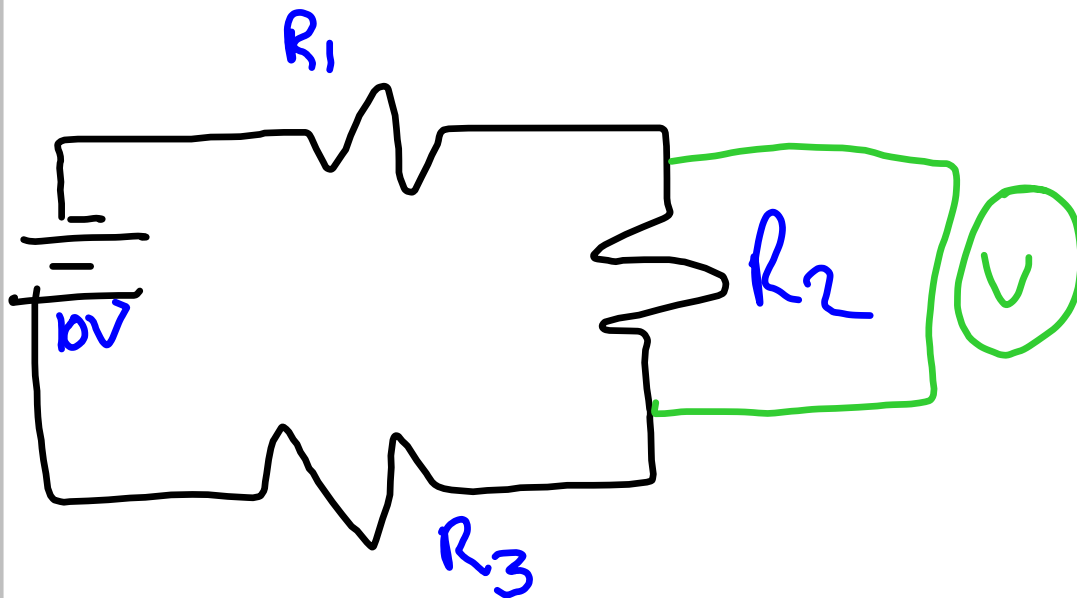In series, Voltage drops occur at each resistor




$$I = 0.0084$$

$$\begin{aligned} V_2 &= I \times R_2 \\ &= 0.0084 \times 330 \\ &= 2.772 \text{ V} \end{aligned}$$

Voltage drops:

$$V_1 + V_2 + V_3 = V_{\text{Total}}$$

Parallel

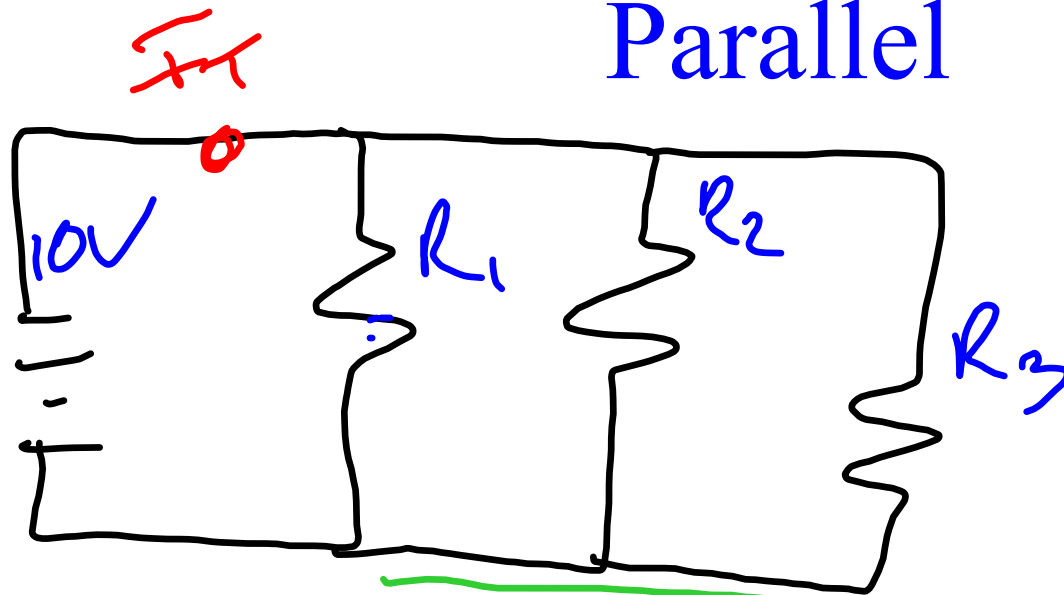

$$R_1 = 330 \Omega$$
$$R_2 = 720 \Omega$$
$$R_3 = 1000 \Omega$$

$$I_1 = \frac{V}{R_1}$$
$$= \frac{10}{330}$$
$$= 0.0303 \text{ A}$$
$$= 30.30 \text{ mA}$$

$$I_T = I_1 + I_2 + I_3$$
$$= 30.3 + 13.8 + 0.001$$
$$= 44.101 \text{ mA}$$

Kirchhoff's
Law


$$I_2 = \frac{10}{720}$$
$$= 0.0138 \text{ A}$$
$$= 13.8 \text{ mA}$$

$$I_3 = \frac{10}{1000}$$
$$= 0.001$$

$$R_T = \frac{V}{I}$$

Parallel
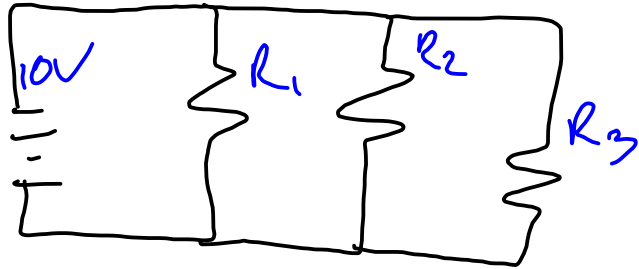
$$\begin{aligned} R_1 &= 330\ \Omega \\ R_2 &= 720\ \Omega \\ R_3 &= 1000\ \Omega \end{aligned}$$



$$\begin{aligned} \frac{1}{R_T} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \\ &= \frac{1}{330} + \frac{1}{720} + \frac{1}{1000} \end{aligned}$$

$$\frac{720 \times 1000 + 330 \cdot 1000 + 330 \times 720}{330 \times 720 \times 1000}$$




$$= \frac{X}{Y} = \frac{1}{2}$$

Plug into
Calc \rightarrow

$$\begin{aligned} &0.00183 \\ \frac{1}{R_T} &= \frac{0.00183}{1} \end{aligned}$$

$$R_T = 2$$


Combination Circuits

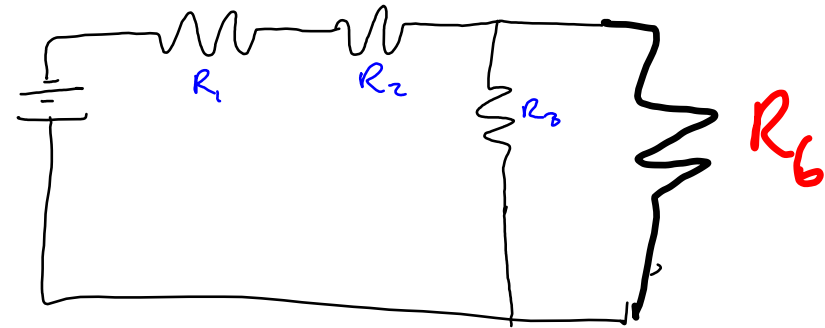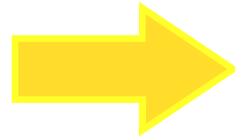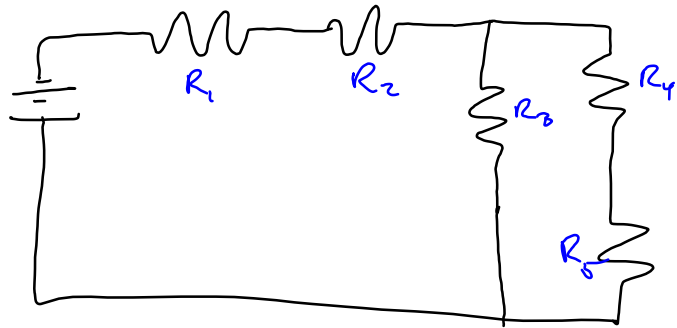


$$R_6 = R_4 + R_5$$



Simple Series

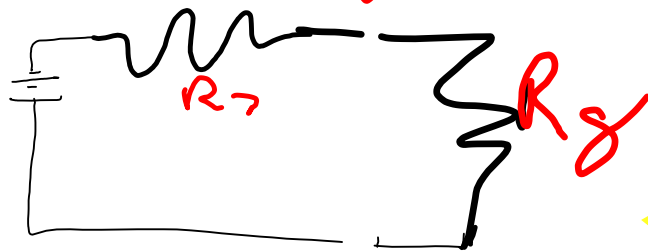

$$R_8 = R_6 + R_3$$

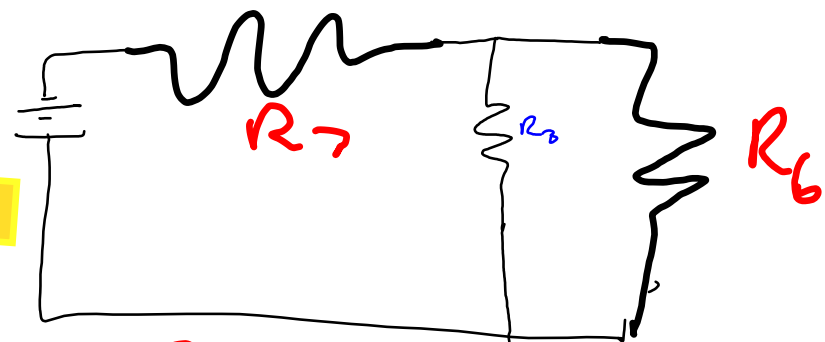

$$R_7 = R_1 + R_2$$

Series

Current static

Voltage drops occur

$$R_T = R_1 + R_2 \dots$$

Parallel

- Current changes at each resistor

- No Voltage drops

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} \dots$$